

# ENEE 132 — Basic Electronics I (Semiconductor Devices)

## **Lecture 4 - Rectifiers**

7 July 2026

- **Part 1 — The DC Power Supply & Half-Wave Rectification**

- The power-supply block diagram and how a half-wave rectifier works
- Average value, the barrier-potential effect, PIV, and transformer coupling

- **Part 2 — Center-Tapped Full-Wave Rectifiers**

- From half-wave to full-wave, and the center-tapped design
- Output voltage, turns ratio, and PIV

- **Part 3 — The Bridge Full-Wave Rectifier**

- Four-diode operation, output voltage, and PIV
- Center-tapped vs. bridge, side by side

- **Part 4 — Wrap-Up**

- Key takeaways and a look ahead to filters and regulators

# Today's Learning Objectives

- **By the End of This Lecture, You Will Be Able To**

- Describe the blocks of a basic dc power supply and what each one does
- Explain half-wave rectification and find the average (DC) value of the output
- Account for the barrier potential and determine the peak output voltage
- Define peak inverse voltage (PIV) and use it to choose a diode rating
- Explain the center-tapped and bridge full-wave rectifiers and analyze their output and PIV
- Compare the center-tapped and bridge designs and choose between them

# Where We Left Off — Why Rectifiers?

## • Recap

- A diode conducts in one direction and blocks the other
- That one-way behaviour is exactly what we need to convert AC into DC

## • The Big Picture

- Wall power is 120 V, 60 Hz AC (230 V, 50 Hz in Ghana); almost every electronic circuit needs steady DC
- A rectifier is the stage that turns AC into pulsating DC
- It is found in every DC power supply — from a phone charger to lab equipment

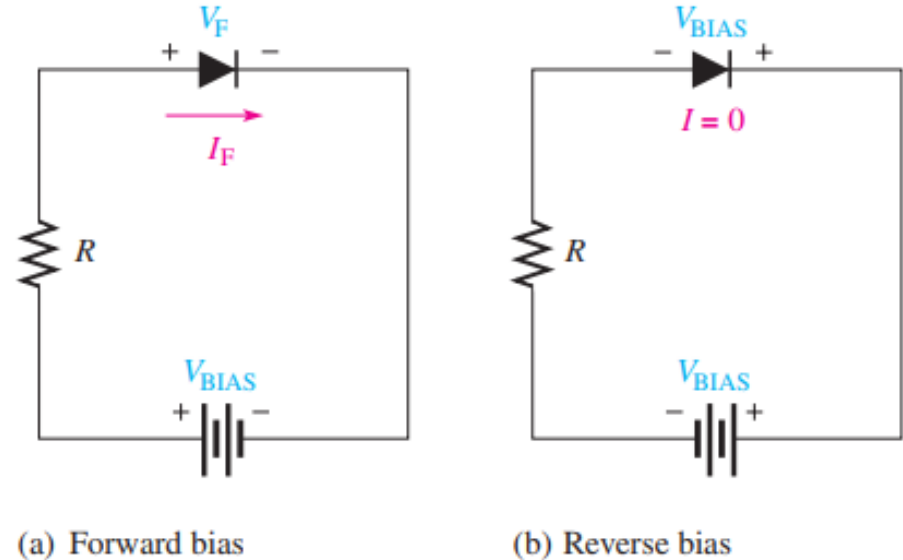


Fig 2.14 — Forward-bias and reverse-bias connections (diode symbol)

# Part 1 — The DC Power Supply & Half-Wave Rectification

# The Basic DC Power Supply


- **From the Wall to Steady DC**

- A DC power supply converts alternating high voltage AC into a constant low voltage DC voltage


- **The Four Stages**

- Transformer — steps the AC voltage up or down (and isolates the circuit)
- Rectifier — converts AC to pulsating DC (half-wave or full-wave)
- Filter — smooths the pulsations into nearly constant DC
- Regulator — holds the DC steady despite changes in line voltage or load
- The load is the circuit powered by the supply

# The Basic DC Power Supply – Visualized

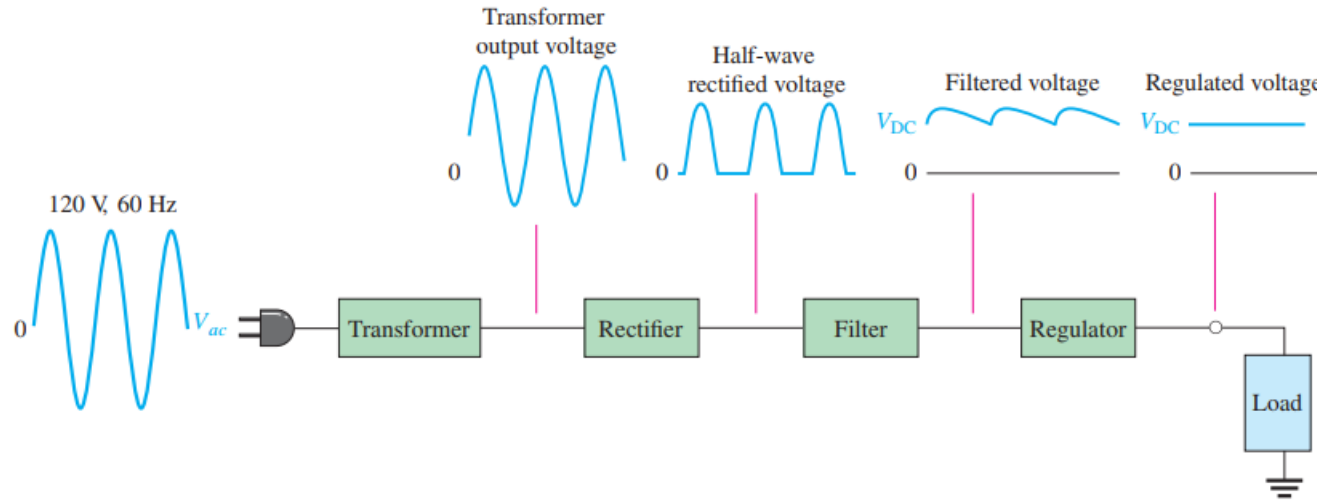

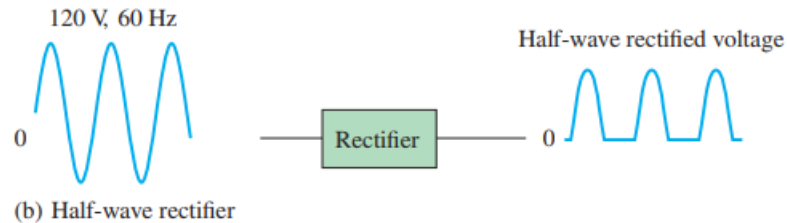(a) Complete power supply with transformer, rectifier, filter, and regulator



(b) Half-wave rectifier

Fig 2.19 — Block diagram of a DC power supply: transformer, rectifier, filter, regulator, load.

# Half-Wave Rectifier Operation

- **The Circuit**

- One diode in series with a load resistor  $R_L$ , driven by an AC source

- **One Cycle (Ideal Diode)**

- Positive half-cycle: the diode is forward-biased and conducts  $\rightarrow$  output follows the input across the load  $R_L$
- Negative half-cycle: the diode is reverse-biased  $\rightarrow$  no current  $\rightarrow$  output is 0 V

- **The Result**

- Only the positive half-cycles reach the load — a pulsating DC voltage at 60 Hz

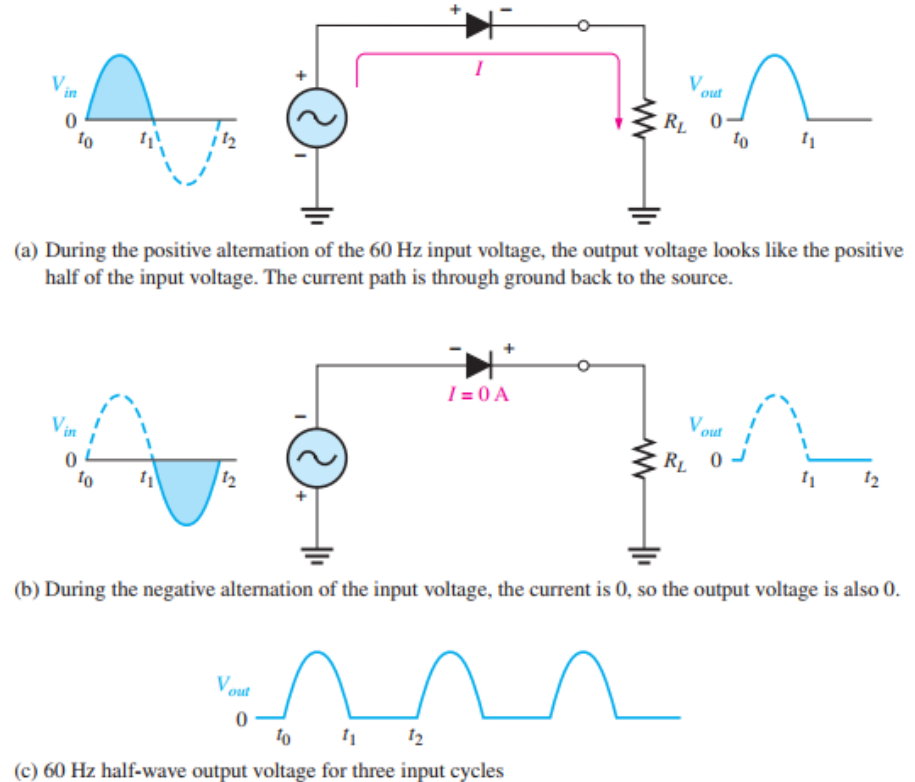


Fig 2.20 — Half-wave rectifier operation using the ideal diode model.



# Average Value of the Half-Wave Output

- **What a DC Voltmeter Reads**

- The average value is the area under the curve over one full cycle, divided by  $2\pi$

- **The Result**

$$V_{\text{AVG}} = \frac{V_p}{\pi}$$

- So the DC value of a half-wave signal is only about 31.8% of its peak

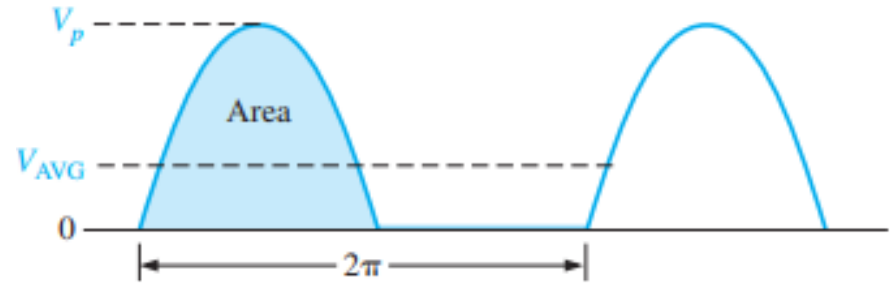


Fig 2.21 — Average value of the half-wave rectified signal.

# Worked Example — Half-Wave Average Value

- **The Question (Example 2-2)**

- A half-wave rectified voltage has peak value  $V_p$ . Find its average (DC) value.

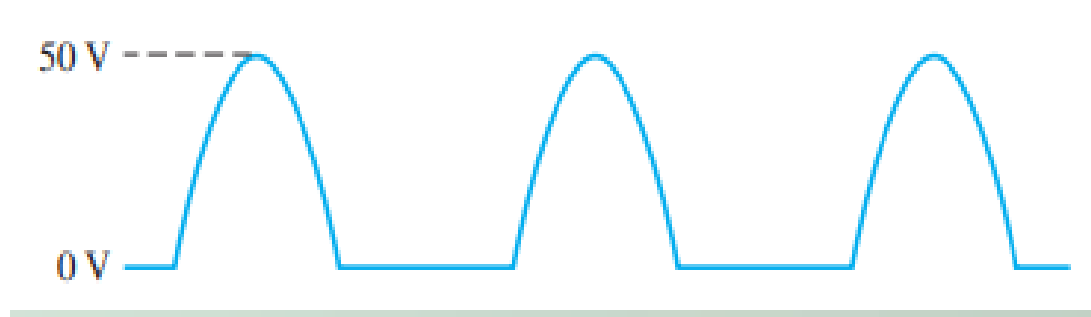


Fig 2.22 — Half-wave rectified waveform for Example 2–2.

- **The Solution**

$$V_{\text{AVG}} = \frac{V_p}{\pi} = \frac{50 \text{ V}}{\pi} = 15.9 \text{ V}$$

- **The Point**

- A DC voltmeter reads only about a third of the peak (31.8% of Peak voltage)

# Effect of the Barrier Potential on the Half-Wave Rectifier Output

- **Using the Practical Model**

- The input must first overcome the diode's 0.7 V barrier before it conducts
- So the output peak is 0.7 V below the input peak:  $V_{p(out)} = V_{p(in)} - 0.7 \text{ V}$

- **Ideal vs. Practical**

- When the peak is much larger than 0.7 V ( $\geq 10 \text{ V}$  rule of thumb), the ideal model is fine
- Example: a 5 V peak  $\rightarrow$  4.3 V (the 0.7 V matters); a 100 V peak  $\rightarrow$  99.3 V (barely matters)

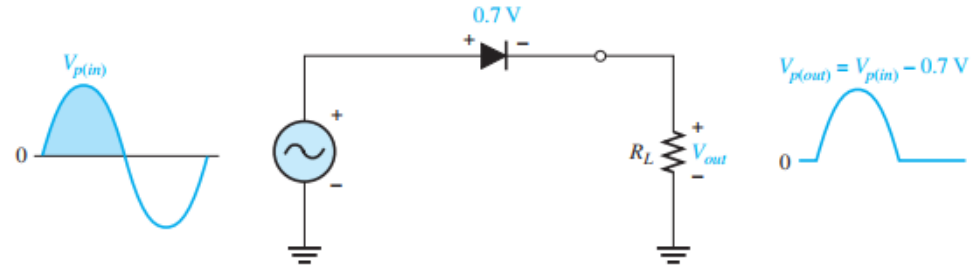


Fig 2.23 — The barrier potential reduces the peak output by about 0.7 V.

## Worked Example — The 0.7 V Drop in Two Cases

### • Example 2–3 — Two Rectifiers, the Same 0.7 V Drop

- Circuit (a): 5 V peak input with a 1N4001 diode
- Circuit (b): 100 V peak input with a 1N4003 diode
- Draw the output voltages of each rectifier for the indicated input voltages

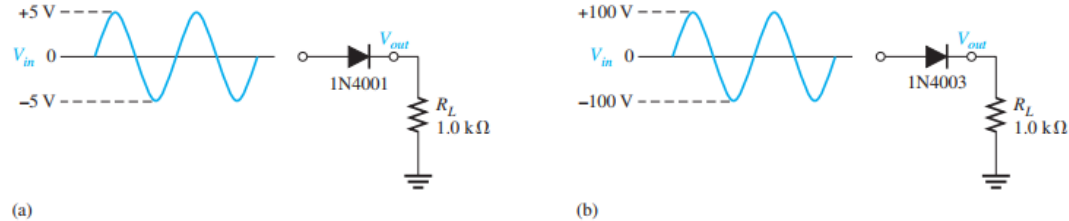


Fig 2.24 — Circuits for Example 2–3 (1N4001 and 1N4003).

### • Solution

- (a)  $V_p(\text{out}) = 5 - 0.7 = 4.30 \text{ V}$
- (b)  $V_p(\text{out}) = 100 - 0.7 = 99.3 \text{ V}$



Fig 2.25 — Output voltages for the circuits

# Peak Inverse Voltage (PIV)

- **The Reverse Stress**

- On each negative half-cycle the diode is reverse-biased and must withstand the input peak
- This maximum repetitive reverse voltage is the peak inverse voltage:  $PIV = V_{p(in)}$

- **Choosing a Diode**

- The diode's reverse-voltage rating must exceed the PIV
- Rule of thumb: the diode should be rated at least 20% higher than the PIV

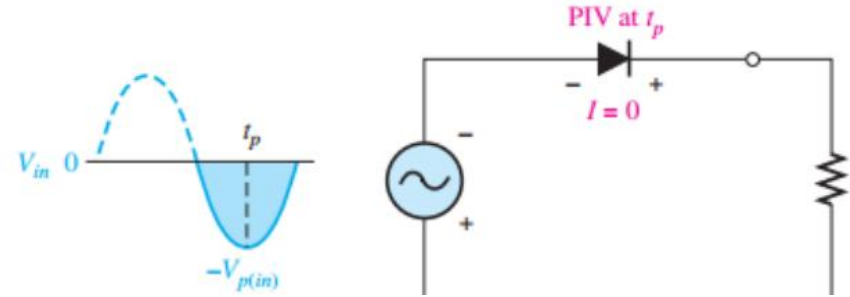


Fig 2.26 — PIV occurs at the negative peak, when the diode is reverse-biased.

# Transformer Coupling

## • Why Use a Transformer

- Steps the AC voltage up or down as needed
- Electrically isolates the rectifier from the wall supply (a safety advantage)

## • Turns Ratio

- Turns ratio  $n = (\text{secondary turns}) / (\text{primary turns})$
- The secondary voltage of a transformer equals the turns ratio,  $n$ , times the primary voltage.
- $V_{sec} = n \cdot V_{pri}$  — so  $n > 1$  it is step-up transformer, if  $n < 1$  it is a step-down transformer. If  $n = 1$ , it is an isolation transformer

## • Rectifier Output

- $V_p(\text{out}) = V_p(\text{sec}) - 0.7 \text{ V}$

## • PIV

- $PIV = V_p(\text{sec})$

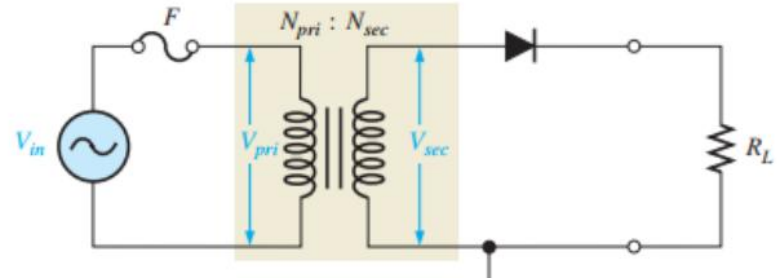


Fig 2.27 — Half-wave rectifier with transformer-coupled input voltage.

# Worked Example — Transformer-Coupled Half-Wave

## • The Question (Example 2-4)

- Determine the peak value of the output voltage for Figure 2–28 if the turns ratio is 0.5.

## • The Solution

- Peak secondary voltage:  $V_p(\text{sec}) = n \cdot V_p(\text{pri}) = 0.5 \times 170 \text{ V} = 85 \text{ V}$
- Peak output (one diode drop):  $V_p(\text{out}) = V_p(\text{sec}) - 0.7 \text{ V} = 85 - 0.7 = 84.3 \text{ V}$

## • Note

- $n < 1$  steps the voltage down; the diode's PIV equals  $V_p(\text{sec}) = 85 \text{ V}$

## • Related Problem

- Determine the peak value of the output voltage for Figure 2–28 if  $n = 2$  and  $V_p(\text{in}) = 312 \text{ V}$ .
- What is the PIV across the diode?
- Describe the output voltage if the diode is turned around.

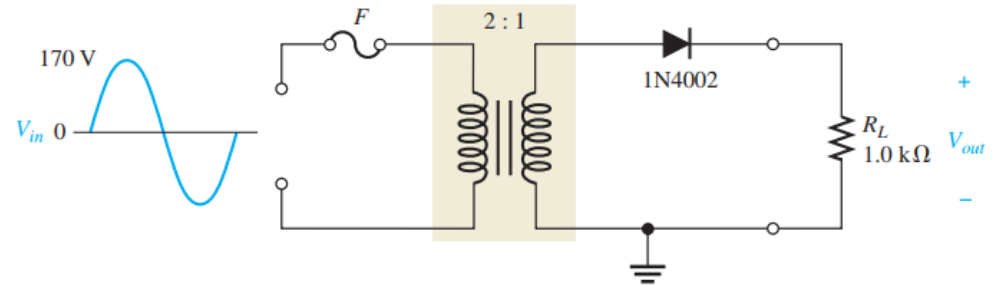


Fig 2.28 — Circuit for Example 2–4.

## Quick Check #1 — Half-Wave Rectification

- **Question 1**

- Name the four stages of a basic dc power supply, in order.

- **Question 2**

- During which half-cycle does a positive half-wave rectifier conduct?

- **Question 3**

- What is the average (DC) value of a half-wave output in terms of  $V_p$ ?

- **Question 4**

- How does the barrier potential change the peak output voltage?

- **Question 5**

- What is PIV, and how does it relate to the input peak?



## Part 2 — Full-Wave Rectifiers

# From Half-Wave to Full-Wave

## • The Idea

- A half-wave rectifier wastes one half of every cycle
- A full-wave rectifier uses BOTH half-cycles — current flows through the load on each one

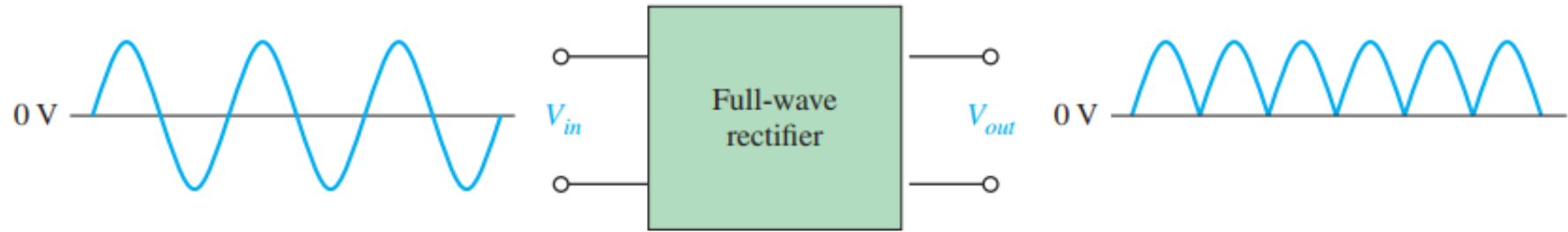


Fig 2.29 — Full-wave rectification: output frequency is twice the input.

## • The Result

- The average (DC) value doubles:

$$V_{AVG} = \frac{2V_p}{\pi}$$

- That's about 63.7% of the peak — twice the half-wave value

# Worked Example — Full-Wave Average Value

- **The Question (Example 2-5)**

- Find the average (DC) value of a full-wave rectified voltage.

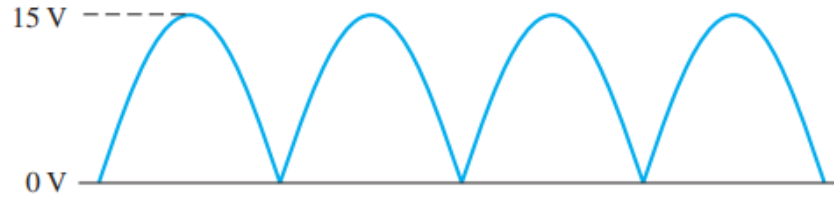


Fig 2.30 — Full-wave rectified waveform for Example 2–5.

- **The Solution**

$$V_{\text{AVG}} = \frac{2V_p}{\pi} = \frac{2(15 \text{ V})}{\pi} = \mathbf{9.55 \text{ V}}$$

- **Compare**

- That's about 63.7% of the peak

# The Center-Tapped Full-Wave Rectifier

## • The Circuit

- A center-tapped rectifier is a type of full-wave rectifier that uses two diodes connected to the secondary of a center-tapped transformer
- Two diodes fed from a center-tapped transformer secondary
- Half of the total secondary voltage appears between the center tap and each end

## • How It Works

- Positive half-cycle: D1 forward-biased, D2 reverse-biased → current through D1 and RL
- Negative half-cycle: D2 forward-biased, D1 reverse-biased → current through D2 and RL
- Current flows the same direction through RL on both halves → full-wave output


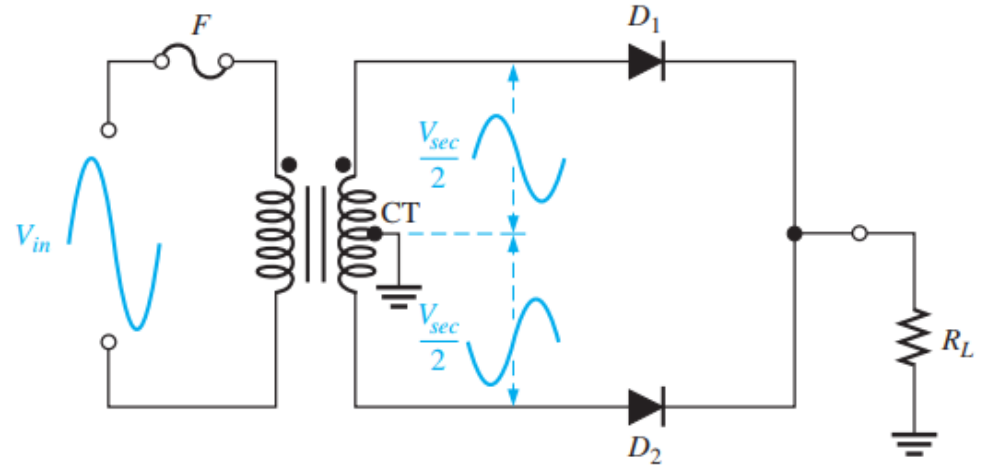


Fig 2.31 — A center-tapped full-wave rectifier.


# Center-Tapped — How It Works
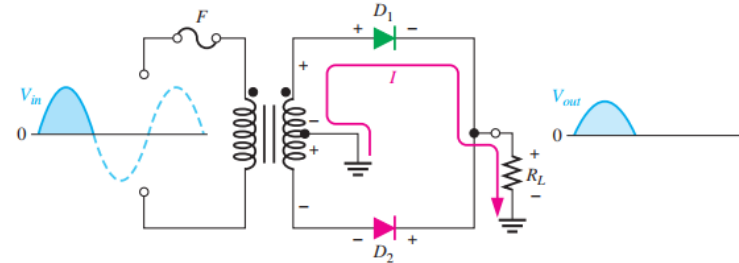
## • Two Diodes Share the Work — One per Half-Cycle

- Positive half-cycle: D1 forward-biased, D2 reverse-biased → current through D1 and RL
- Negative half-cycle: D2 forward-biased, D1 reverse-biased → current through D2 and RL
- In BOTH half-cycles the load current is in the same direction → a full-wave output
- Each half-cycle delivers a pulse, so the output frequency is twice the input



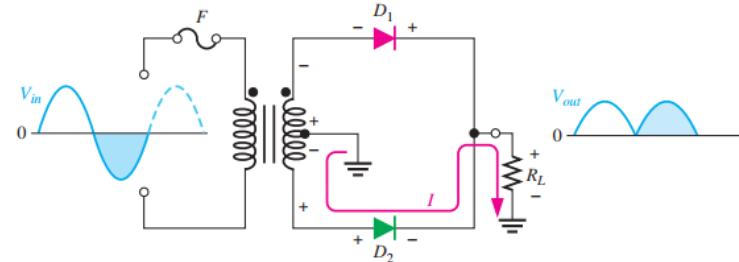(a) During positive half-cycles,  $D_1$  is forward-biased and  $D_2$  is reverse-biased.



(b) During negative half-cycles,  $D_2$  is forward-biased and  $D_1$  is reverse-biased.

Fig 2.32 — Operation of a center-tapped rectifier over both half-cycles.

# Center-Tapped — Effect of Turns Ratio on the Output Voltage

- **With  $n = 1$  (an Isolation Transformer)**

- The total secondary voltage equals the primary:  $V_p(\text{sec}) = V_p(\text{pri})$
- Only HALF the secondary drives each diode path:  $V_p(\text{sec})/2$
- So the peak output is:  $V_p(\text{out}) = V_p(\text{pri})/2 - 0.7 \text{ V}$

- **Why This Matters**

- A turns ratio of 1 gives an output near half the input — to recover the full input peak you step up (next slide,  $n = 2$ )

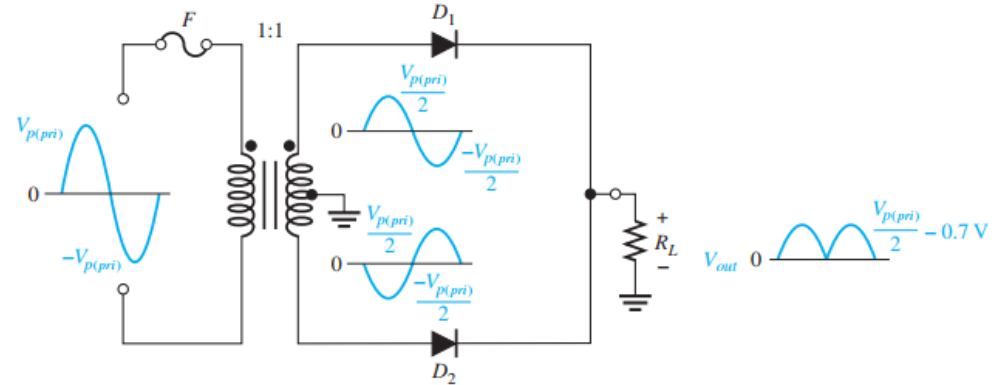


Fig 2.33 — Center-tapped rectifier with a transformer turns ratio of 1.

# Center-Tapped: Output Voltage & Turns Ratio

## • The Output Rule

- The output is always half the total secondary voltage, less one diode drop:

$$V_{out} = \frac{V_{sec}}{2} - 0.7 \text{ V}$$

## • Turns-Ratio Examples

- $n = 1$ : each half of the secondary gets half the primary peak
- $n = 2$  (step-up): the total secondary is twice the primary, so each half equals the primary peak

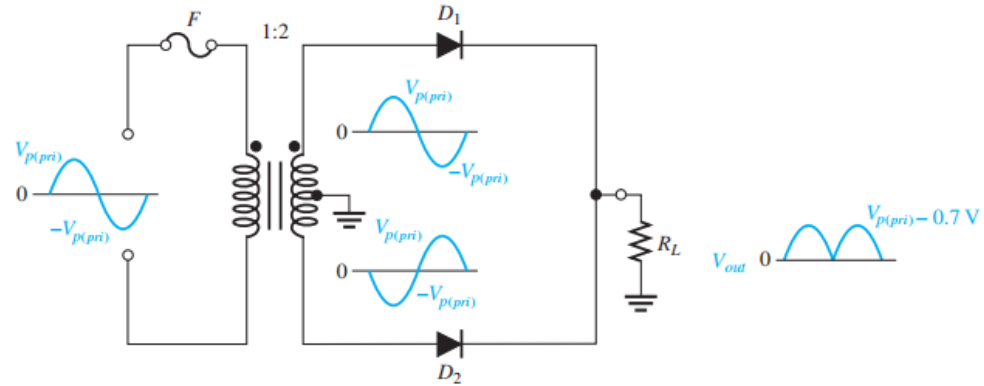


Fig 2.34 — Center-tapped rectifier with a transformer turns ratio of 2.

# Center-Tapped: Peak Inverse Voltage

- **The Reverse Stress**

- Each diode alternates between forward- and reverse-biased
- The reverse-biased diode must withstand nearly the full secondary voltage

- **The Formula**

- The peak inverse voltage across D2 is

$$\begin{aligned} \text{PIV} &= \left( \frac{V_{p(sec)}}{2} - 0.7 \text{ V} \right) - \left( -\frac{V_{p(sec)}}{2} \right) = \frac{V_{p(sec)}}{2} + \frac{V_{p(sec)}}{2} - 0.7 \text{ V} \\ &= V_{p(sec)} - 0.7 \text{ V} \end{aligned}$$

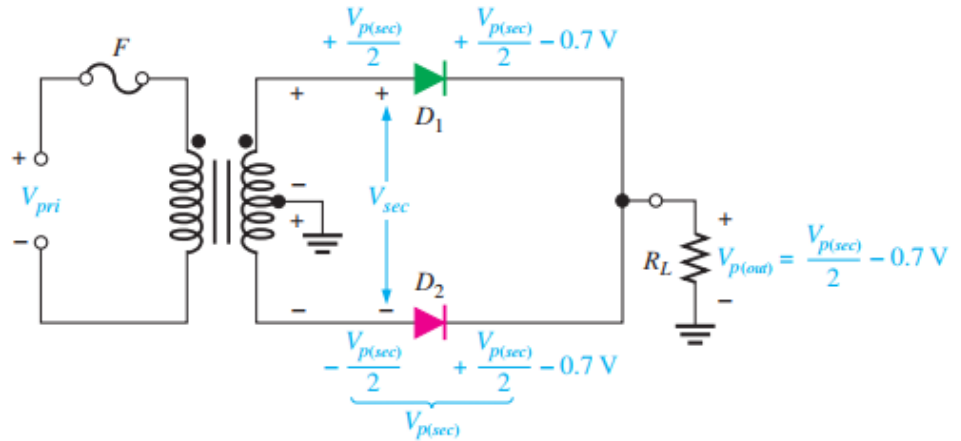


Fig 2.35 — Diode reverse voltage (D2 reverse-biased, D1 forward-biased).

- The PIV across either diode in a full-wave center-tapped rectifier is

$$\text{PIV} = 2V_{p(out)} + 0.7 \text{ V}$$



# Worked Example — Center-Tapped Rectifier

## • The Question (Example 2-6)

- (a) Show the voltage waveforms across each half of the secondary winding and across  $R_L$  when a 100 V peak sine wave is applied to the primary winding in Figure 2–36.
- (b) Assuming a 20% margin, what minimum PIV rating must the diodes have?

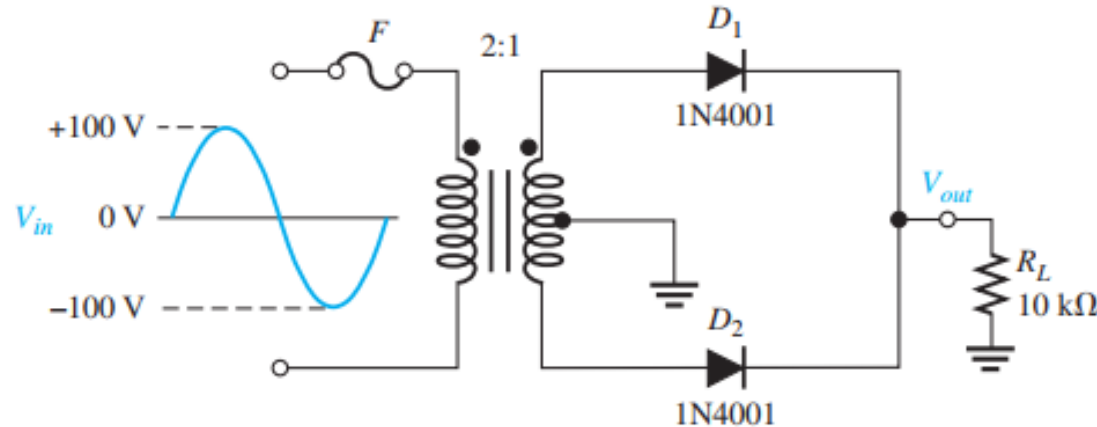


Fig 2.36 — Circuit for Example 2–6.

## Worked Example — Solution

- **(a) Example 2–6 — 100 V Peak Input,  $n = 0.5$**

- Total peak secondary:  $V_p(\text{sec}) = 0.5 \times 100 = 50 \text{ V}$
- Across each half of the secondary:  $50 / 2 = 25 \text{ V peak}$
- Peak load output:  $V_p(\text{out}) = 25 - 0.7 = 24.3 \text{ V}$

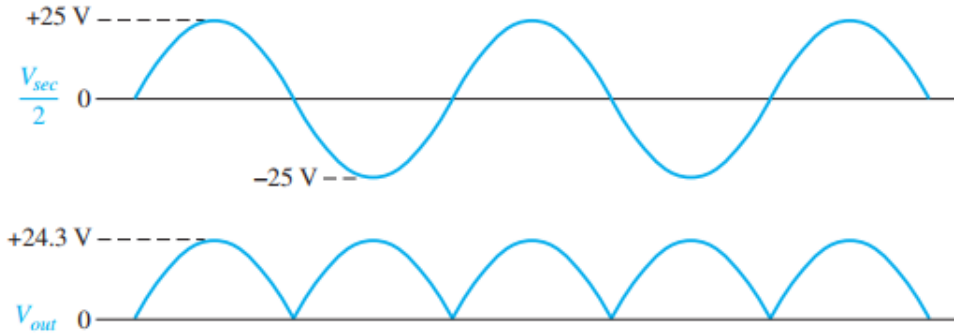


Fig 2.37 — Output waveforms for Example 2–6.

- **(b) Required Diode PIV**

- $PIV = 2 \cdot V_p(\text{out}) + 0.7 = 2(24.3) + 0.7 = 49.3 \text{ V}$
- With a 20% margin, choose diodes rated at least 60 V

## Quick Check #2 — Full-Wave & Center-Tapped

- **Question 1**

- What is the average (dc) value of a full-wave output in terms of  $V_p$ ?

- **Question 2**

- In a center-tapped rectifier, which diode conducts on the positive half-cycle?

- **Question 3**

- Write the output-voltage formula for a center-tapped rectifier.

- **Question 4**

- Write the PIV formula for a center-tapped rectifier.

- **Question 5**

- Why does a full-wave output have twice the dc value of a half-wave output?

# Part 3 — The Bridge Rectifier


# The Bridge Full-Wave Rectifier

## • The Circuit


- The bridge rectifier uses four diodes arranged in a bridge — no center-tapped transformer needed
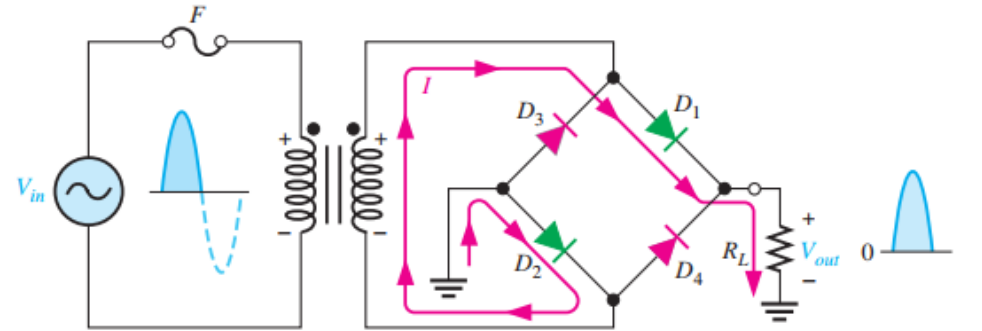
## • How It Works

- Positive half-cycle:  $D_1$  and  $D_2$  are forward biased and conduct ( $D_3$ ,  $D_4$  off) → output across  $R_L$
- Negative half-cycle:  $D_3$  and  $D_4$  are forward biased and conduct ( $D_1$ ,  $D_2$  off) → current the same direction through  $R_L$
- Both halves drive the load the same way → full-wave output



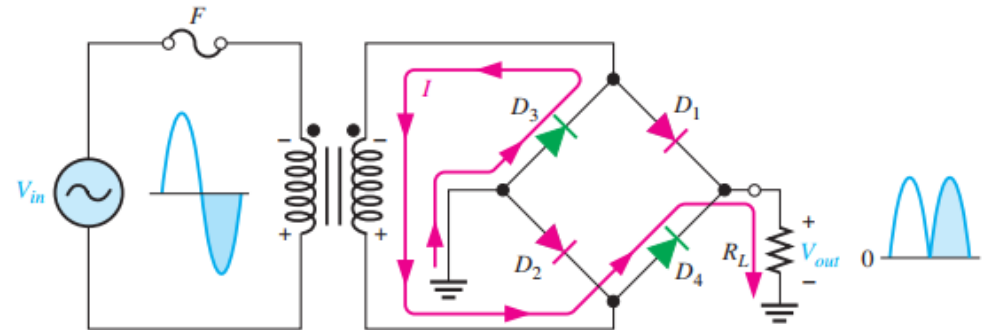(a) During the positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased.



(b) During the negative half-cycle of the input,  $D_3$  and  $D_4$  are forward-biased and conduct current.  $D_1$  and  $D_2$  are reverse-biased.

Fig 2.38 — Operation of a bridge rectifier over both half-cycles.

# Bridge: Output Voltage

- **Two Diodes in the Path**

- On each half-cycle, two diodes are in series with the load
- So two diode drops ( $2 \times 0.7 \text{ V}$ ) come off the secondary peak:  
$$V_{p(out)} = V_{p(sec)} - 1.4 \text{ V}$$

- **Compared to Center-Tapped**

- The bridge uses the FULL secondary voltage (not half), so no step-up transformer is needed for the same output


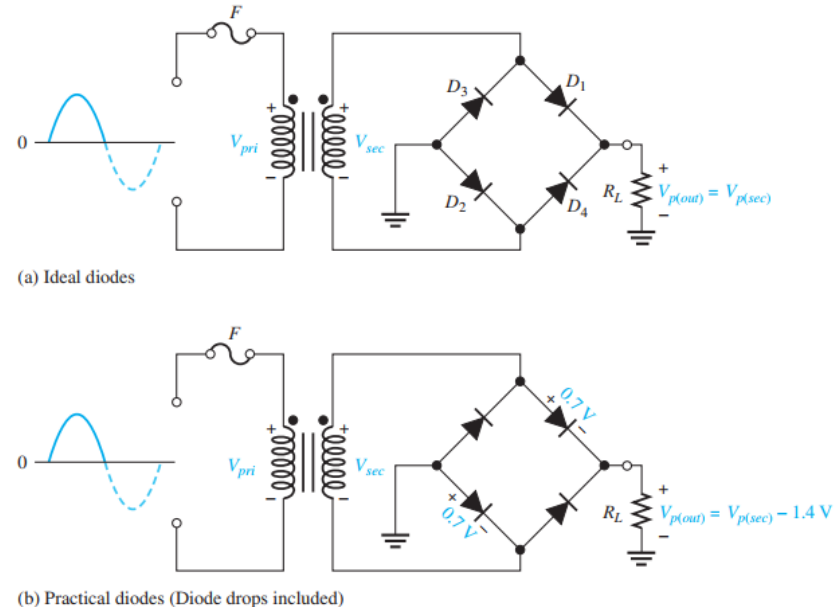


Fig 2.39 — Bridge operation during a positive half-cycle.


# Bridge: Peak Inverse Voltage
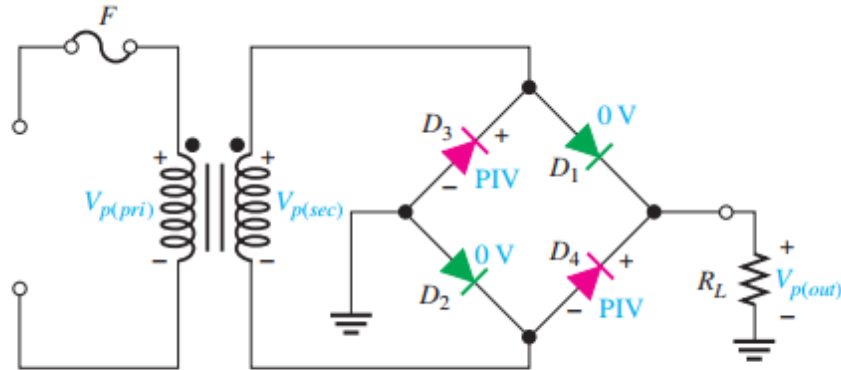
## • The Reverse Stress

- Each reverse-biased diode sees the peak secondary voltage
- In terms of the output:  $PIV = V_{p(out)} + 0.7 \text{ V}$



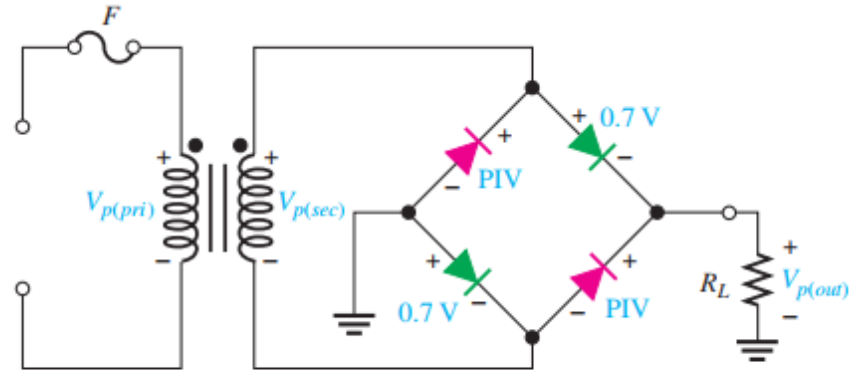(a) For the ideal diode model (forward-biased diodes  $D_1$  and  $D_2$  are shown in green),  $PIV = V_{p(out)}$ .



(b) For the practical diode model (forward-biased diodes  $D_1$  and  $D_2$  are shown in green),  $PIV = V_{p(out)} + 0.7 \text{ V}$ .

Fig 2.40 — Peak inverse voltage across  $D_3$  and  $D_4$  in a bridge rectifier.

## • The Big Advantage

- That's about HALF the PIV of a center-tapped rectifier for the same output voltage
- So bridge diodes can have a lower voltage rating

# Worked Example — Bridge Rectifier

## • The Question (Example 2-7)

- Determine the peak output voltage for the bridge rectifier in Figure 2–41. Assuming the practical model, what PIV rating is required for the diodes? The transformer is specified to have a 12 V rms secondary voltage for the standard 120 V across the primary.

## • The Solution

- Secondary peak:  $V_p(\text{sec}) = 1.414 \times 12 \text{ V} = 17 \text{ V}$
- Output peak:  $V_p(\text{out}) = V_p(\text{sec}) - 1.4 \text{ V} = 17 - 1.4 = 15.6 \text{ V}$
- $\text{PIV} = V_p(\text{out}) + 0.7 \text{ V} = 15.6 + 0.7 = 16.3 \text{ V}$   
→ the diode rating must exceed this

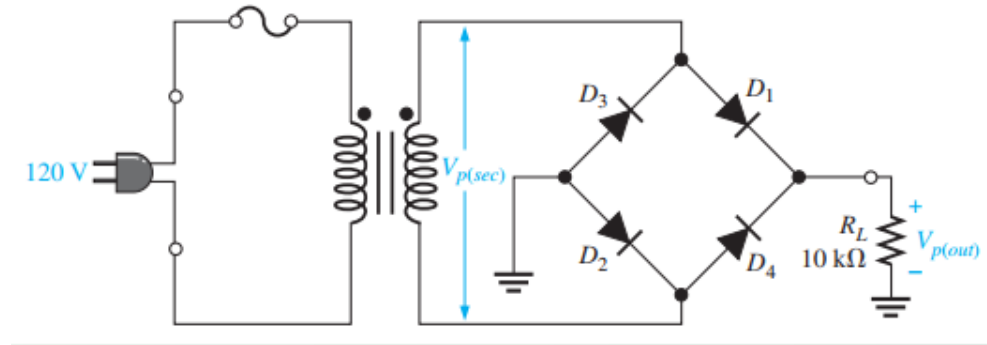


Fig 2.41 — Circuit for Example 2–7 (12 V rms secondary).



# Center-Tapped vs. Bridge — Side by Side

- **Center-Tapped**

- Two diodes + a center-tapped transformer
- Output:  $V_p(\text{out}) = V_p(\text{sec})/2 - 0.7 \text{ V}$  (uses half the secondary, one diode drop)
- $\text{PIV} = 2V_p(\text{out}) + 0.7 \text{ V}$  — higher reverse stress on each diode

- **Bridge**

- Four diodes, an ordinary (non-tapped) transformer
- Output:  $V_p(\text{out}) = V_p(\text{sec}) - 1.4 \text{ V}$  (uses the full secondary, two diode drops)
- $\text{PIV} = V_p(\text{out}) + 0.7 \text{ V}$  — about half the center-tapped value

- **The Trade-Off**

- Bridge: two more diodes and an extra diode drop, but lower PIV and no center tap — the most common choice

## Quick Check #3 — Bridge & Comparison

- **Question 1**

- How many diodes does a bridge rectifier use, and how many conduct at once?

- **Question 2**

- Write the bridge output-voltage formula (practical model).

- **Question 3**

- Write the bridge PIV formula.

- **Question 4**

- For the same output, how does the bridge PIV compare with the center-tapped PIV?

- **Question 5**

- Name one advantage and one disadvantage of the bridge versus the center-tapped design.

# Part 4 — Wrap-Up

## Key Takeaways from Today

- A dc power supply has four stages: transformer → rectifier → filter → regulator → (load)
- Half-wave: uses one half-cycle;  $V_{AVG} = V_p/\pi \approx 0.318 V_p$ ; pulses at 60 Hz
- Practical model:  $V_p(\text{out}) = V_p(\text{in}) - 0.7 \text{ V}$ ;  $PIV = V_p(\text{in})$ , and rate the diode  $\sim 20\%$  higher
- Full-wave: uses both half-cycles;  $V_{AVG} = 2V_p/\pi \approx 0.637 V_p$ ; pulses at 120 Hz
- Center-tapped: 2 diodes;  $V_p(\text{out}) = V_p(\text{sec})/2 - 0.7 \text{ V}$ ;  $PIV = 2V_p(\text{out}) + 0.7 \text{ V}$
- Bridge: 4 diodes;  $V_p(\text{out}) = V_p(\text{sec}) - 1.4 \text{ V}$ ;  $PIV = V_p(\text{out}) + 0.7 \text{ V}$  — about half the center-tapped PIV
- Transformer coupling sets the voltage ( $V_{\text{sec}} = n \cdot V_{\text{pri}}$ ) and provides isolation

## Coming Up — Week 5: Filters & Voltage Regulators

- **Next Topic — Power-Supply Filters & Regulators (Lecture Notes pp. 66–74)**

- Smoothing pulsating dc with a capacitor-input filter
- Ripple voltage and the ripple factor
- Voltage regulation against line and load changes

- **To Prepare**

- Be comfortable finding the peak output of a rectifier — we'll filter that output
- Recall the difference between half-wave (60 Hz) and full-wave (120 Hz) ripple

- **Reminder**

- Read pp. 66–74 before class

Thank You — Questions?