

ENEE 132 — Basic Electronics I (Semiconductor Devices)

Lecture 6 - The Zener Diode & Applications

14 July 2026

- **Part 1 — The Zener Diode**

- What it is, the two kinds of breakdown, and the V-I characteristic
- The equivalent circuit, temperature coefficient, and power derating

- **Part 2 — Zener Voltage Regulation**

- Regulating against a varying input voltage and a varying load
- From no load to full load, with worked examples

- **Part 3 — Wrap-Up**

- When to use for a zener, key takeaways, and a look ahead to special-purpose diodes

Today's Learning Objectives

- **By the End of This Lecture, You Will Be Able To**

- Recognize a zener diode and explain why it operates in reverse breakdown
- Distinguish zener breakdown from avalanche breakdown
- Read the zener V-I characteristic and identify V_Z , I_{ZK} , and I_{ZM}
- Use the ideal and practical (Z_Z) equivalent circuits
- Apply the temperature coefficient and power derating to find V_Z and $P_D(\max)$
- Analyze zener regulation for a varying input voltage and a varying load

Part 1 — The Zener Diode

Where We Left Off — Why a Zener Diode?

- **V-I Characteristic of a Diode**

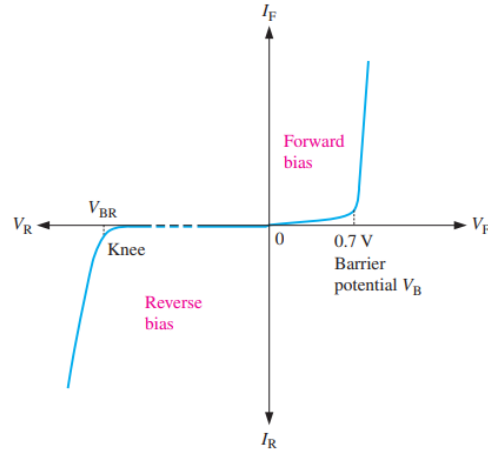


Fig 2.12 — The complete V-I characteristic curve for a diode

- **The Zener Diode Idea**

- An ordinary diode avoids breakdown; the zener is built to operate in that region on purpose
- That flat breakdown voltage becomes a stable reference we can regulate with
- Main uses: voltage references and regulators in power supplies, voltmeters, and instruments

What Is a Zener Diode?

- **A Diode Built for Breakdown**

- A Zener diode is a silicon pn junction device that is designed to operate in the reverse-breakdown region
- Its breakdown voltage (V_z) is set precisely by controlling the doping during manufacture

- **The Symbol**

- Like a diode, but with a bent cathode line shaped like a 'Z' (for zener)
- In breakdown, the voltage across it stays almost constant even as the current changes

- **Important Note**

- In reverse breakdown, the voltage across it stays almost constant even as the current changes drastically – this is key to the Zener diode operation



Fig 3.1 — Zener diode schematic symbol (cathode K, anode A).

The Zener V-I Characteristic

- **Operating Region of Zener Diode**

- In Forward Bias, it behaves like an ordinary diode
- The action is in the reverse-breakdown region (the shaded operating area)

- **The Key Feature**

- Once in breakdown, V_Z is nearly vertical: large current swings produce only a tiny voltage change
- That near-constant voltage is what makes it a regulator

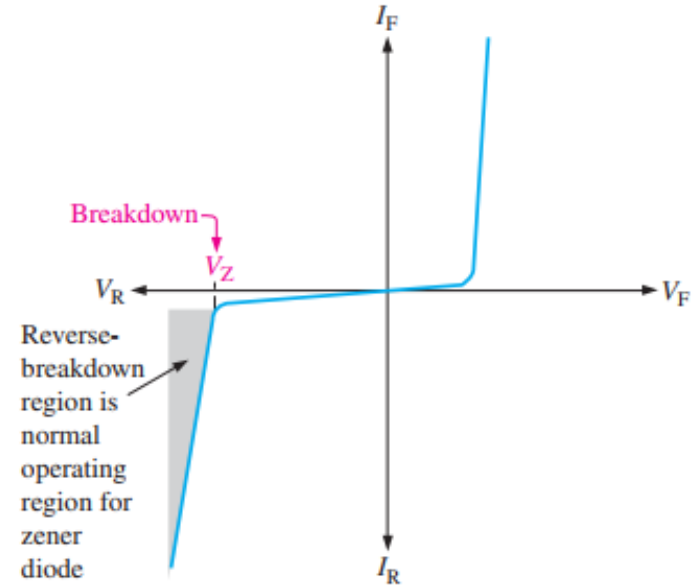


Fig 3.2 — General zener V-I characteristic; the shaded reverse-breakdown region is the operating region.

Two Types of Reverse Breakdown

- **Zener Breakdown (Low Reverse Voltage)**

- Heavy doping makes a very thin depletion region with an intense electric field
- The intense electric field pulls electrons loose directly — dominant below about 5 V

- **Avalanche Breakdown (High Reverse Voltage)**

- The collision-multiplication effect which occurs at high reverse voltages — dominant above about 5 V

- **Operating Voltages**

- Zener Diodes are commercially available with breakdown voltages from less than 1 V to more than 250 V with specified tolerances from 1% to 20%.

Breakdown Characteristics — I_{ZK} , I_{ZM} , V_Z

• Reading the Reverse Curve

- Reverse current is extremely small until the knee; in breakdown it's called the zener current, I_Z
- The internal Zener resistance is also called Zener impedance (Z_Z)
- At breakdown, the Zener impedance decreases as the reverse current increases rapidly
- V_Z stays essentially constant from the knee up (rising only slightly as I_Z increases)

• The Two Limits That Bracket Regulation

- I_{ZK} — the knee (minimum) current; below it, the voltage collapses and regulation is lost
- I_{ZM} — the maximum current; above it, power dissipation can destroy the diode
- So the zener regulates for any I_Z between I_{ZK} and I_{ZM} ; V_Z is quoted at a test current I_Z


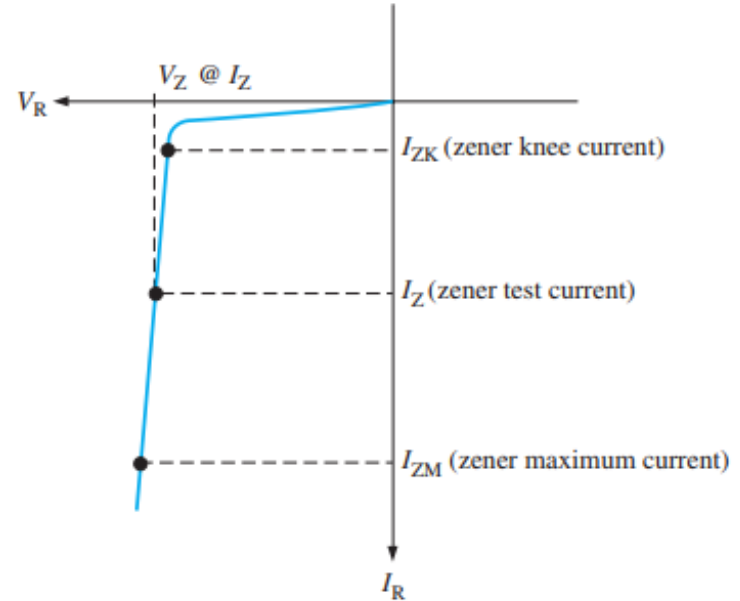


Fig 3.3 — Reverse characteristic: I_{ZK} at the knee, test current I_Z , and maximum I_{ZM} .


Zener Equivalent Circuits

• Ideal Model (First Approximation)

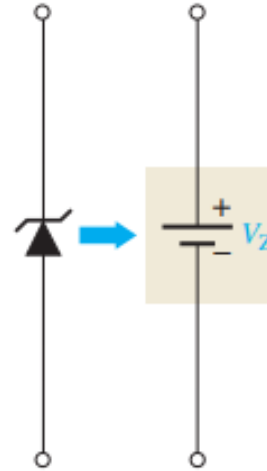- In reverse breakdown the zener holds an almost constant voltage equal to V_Z
- The ideal model replaces the zener with a constant DC voltage source (a battery symbol — though it generates nothing)
- The characteristic curve is treated as a vertical line at V_Z



(a) Ideal model

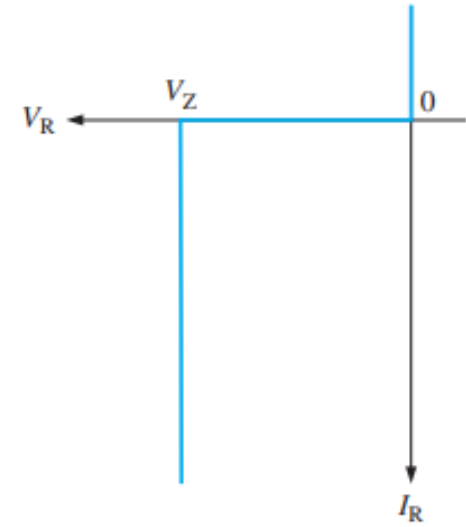

(b) Ideal characteristic curve

Fig 3.4 — Ideal zener model: a constant V_Z and a vertical characteristic curve.


The Practical Zener Model (Second Approximation)

• The Curve Isn't Perfectly Vertical


- A small current change ΔI_Z produces a small voltage change ΔV_Z
- Zener impedance (by Ohm's law):

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

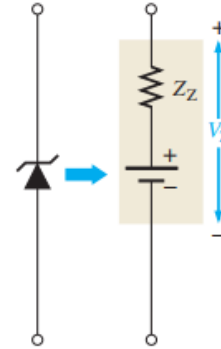- Z_Z is specified at the test current; treat it as a small, roughly constant resistance
- Avoid operating near the knee, where the impedance changes dramatically in that area



(a) Practical model

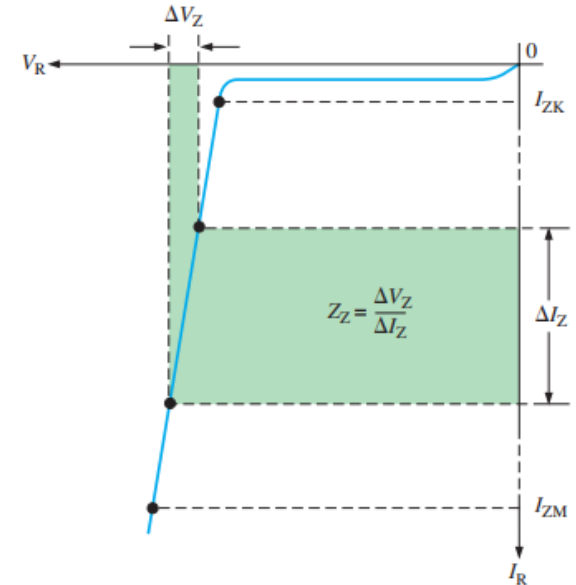

(b) Characteristic curve. The slope is exaggerated for illustration.

Fig 3.5 — Practical model: the impedance Z_Z gives the characteristic a slight slope.

Worked Example — Zener Impedance Z_Z

• Example 3–1

- A zener diode exhibits a certain change in V_Z for a certain change in I_Z on a portion of the linear characteristic curve between I_{ZK} and I_{ZM} as illustrated in Figure 3–6. What is the zener impedance?

• Solution

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{50 \text{ mV}}{5 \text{ mA}} = 10 \, \Omega$$

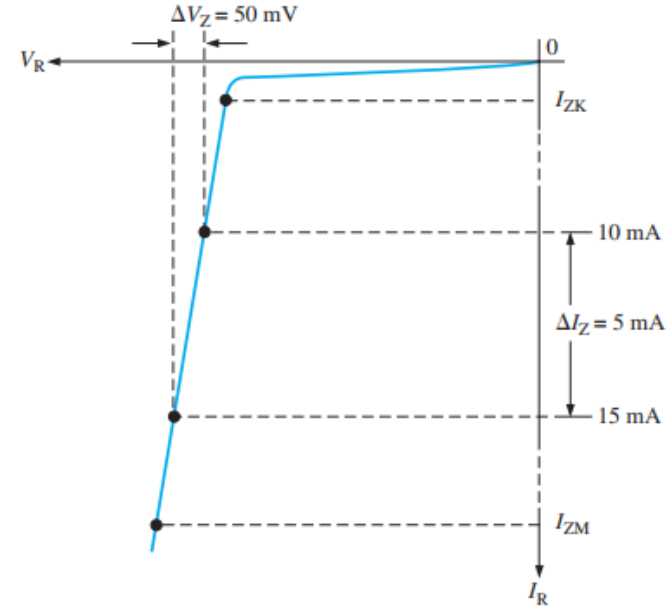


Fig 3.6 — A change ΔV_Z over ΔI_Z on the linear region gives Z_Z .

Temperature Coefficient

• Vz Drifts with Temperature

- The formula for calculating the change in Zener voltage for a given junction temperature change, for a specified temperature coefficient is

$$\Delta V_Z = V_Z \times TC \times \Delta T$$

- V_Z is the nominal Zener voltage at the reference temperature of 25°C
- TC is the temperature coefficient which coefficient specifies the percent change in Zener voltage for each degree Celsius change in temperature
- ΔT is the change in temperature from the reference temperature

• Sign of TC

- Positive TC: V_Z rises as temperature rises
- Negative TC: V_Z falls as temperature rises
- In some cases, the temperature coefficient is expressed in mV/°C rather than in %/°C. For these cases, the change in Zener voltage is

$$\Delta V_Z = TC \times \Delta T$$

Worked Example — Temperature Coefficient

An 8.2 V zener diode (8.2 V at 25°C) has a positive temperature coefficient of 0.05%/°C. What is the zener voltage at 60°C?

Solution The change in zener voltage is

$$\begin{aligned}\Delta V_Z &= V_Z \times TC \times \Delta T = (8.2 \text{ V})(0.05\%/^{\circ}\text{C})(60^{\circ}\text{C} - 25^{\circ}\text{C}) \\ &= (8.2 \text{ V})(0.0005/^{\circ}\text{C})(35^{\circ}\text{C}) = 144 \text{ mV}\end{aligned}$$

Notice that 0.05%/°C was converted to 0.0005/°C. The zener voltage at 60°C is

$$V_Z + \Delta V_Z = 8.2 \text{ V} + 144 \text{ mV} = \mathbf{8.34 \text{ V}}$$

Zener Power Dissipation and Derating

- **How Much Power can a Zener Diode Handle**

- Zener Diodes are specified to operate at a maximum power called the maximum DC power dissipation

$$P_D = V_Z I_Z$$

- Datasheets give a maximum, $P_{D(max)}$ (e.g. 500 mW for a 1N746 Zener Diode, up to tens of watts for big ones)

- **Power Derating**

- The maximum power dissipation of a Zener diode is specified for temperatures at or below a certain value (e.g., 50 °C)
- Above a specified temperature, $P_{D(max)}$ drops by a derating factor (in mW/°C)
- The maximum derated power can be determined by

$$P_{D(derated)} = P_{D(max)} - (mW/^\circ C) \Delta T$$

Worked Example — Power Derating

- **The Question (Example 3-3)**

- A certain zener diode has a maximum power rating of 400 mW at 50°C and a derating factor of 3.2 mW/°C. Determine the maximum power the zener can dissipate at a temperature of 90°C.

- **The Solution**

- Temperature above rating: $\Delta T = 90 - 50 = 40^\circ\text{C}$
- Reduction = $3.2 \text{ mW}/^\circ\text{C} \times 40^\circ\text{C} = 128 \text{ mW}$
- Derated power = $400 \text{ mW} - 128 \text{ mW} = \mathbf{272 \text{ mW}}$

- **Related Problem**

- A certain 50W zener diode must be derated with a derating factor of 0.5mW/°C above 75°C. Determine the maximum power it can dissipate at 160°C.

Quick Check #1 — The Zener Diode

- **Question 1**

- What region is a zener diode designed to operate in, and what sets its breakdown voltage?

- **Question 2**

- Which breakdown type dominates below ~ 5 V, and which above?

- **Question 3**

- What do I_{ZK} and I_{ZM} represent, and why does regulation require staying between them?

- **Question 4**

- Write the definition of zener impedance Z_z .

- **Question 5**

- If a zener has a positive temperature coefficient, what happens to V_z as it heats up?

Part 2 — Zener Voltage Regulation


Zener Regulation with a Variable Input Voltage

• The Circuit


- A series current-limiting resistor R feeds the zener; the load sits across the zener
- As V_{IN} rises and falls (within limits), the zener holds the output near V_Z

• What Moves

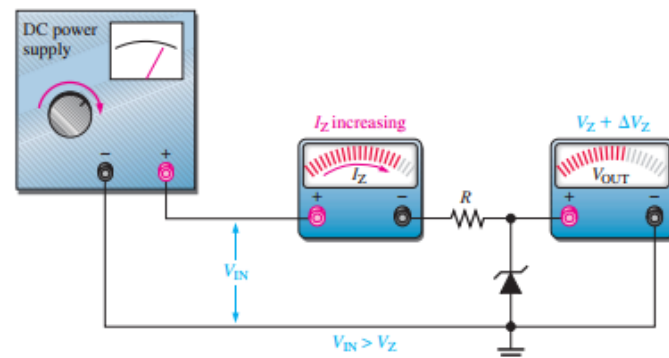- When V_{IN} changes, the zener current I_Z changes proportionally to absorb it
- The input range is bounded by I_{ZK} (at the low end) and I_{ZM} (at the high end)
- Zener regulators are simple but inefficient — best for low-current loads



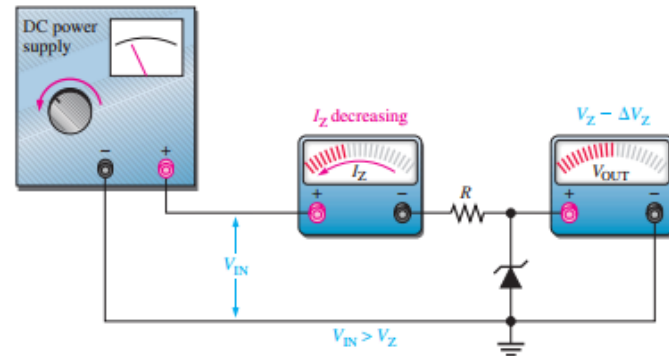(a) As the input voltage increases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).



(b) As the input voltage decreases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).

Fig 3.9 — Zener regulation as the input voltage varies.

Worked Example — Input-Voltage Range

• The Question

- A 10 V zener (1N4740A): $I_{ZK} = 0.25 \text{ mA}$, $P_{D(\max)} = 1 \text{ W}$, with a 220Ω series resistor. Over what input range does it regulate?

• The Solution

- Max current: $I_{ZM} = P_{D(\max)} / V_Z = 1 \text{ W} / 10 \text{ V} = 100 \text{ mA}$
- At I_{ZK} : $V_R = 0.25 \text{ mA} \times 220 \Omega = 0.055 \text{ V}$
 $V_{IN(\min)} = 10 + 0.055 = 10.055 \text{ V}$
- At I_{ZM} : $V_R = 100 \text{ mA} \times 220 \Omega = 22 \text{ V}$
 $V_{IN(\max)} = 10 + 22 = 32 \text{ V}$
- So it holds $\sim 10 \text{ V}$ out for any input from 10.055 V to 32 V

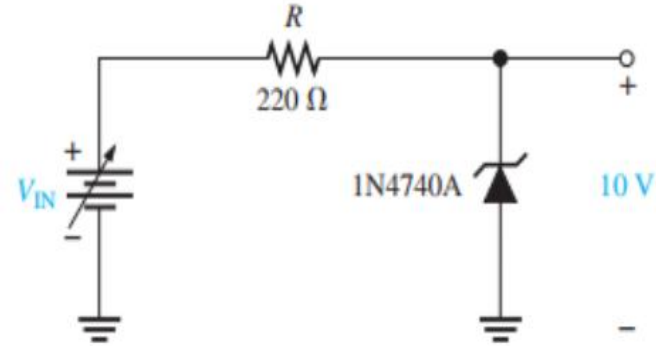


Fig 3.10 — Regulator circuit for the input-range analysis (1N4740A, ideal model).

Worked Example — Input Range Including Z_z

• Example 3–5

- Determine the minimum and the maximum input voltages that can be regulated by the Zener diode
- Information from datasheet for a 1N4733A Zener Diode: $V_z = 5.1\text{V}$ at $I_z = 49\text{ mA}$, $I_{zk} = 1\text{ mA}$, and $Z_z = 7\ \Omega$ at I_z

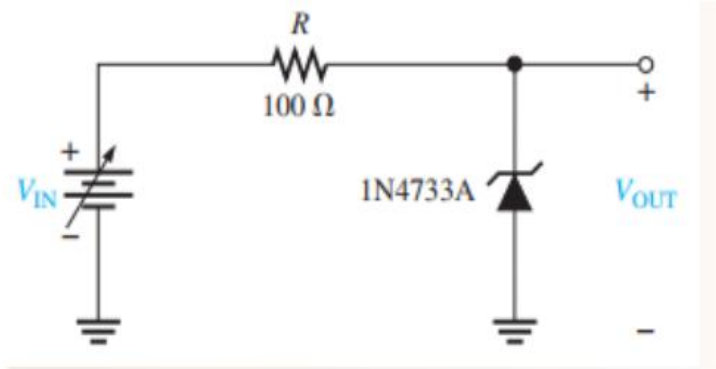


Fig 3.11 — Zener regulator for Example 3–5 (1N4733A).

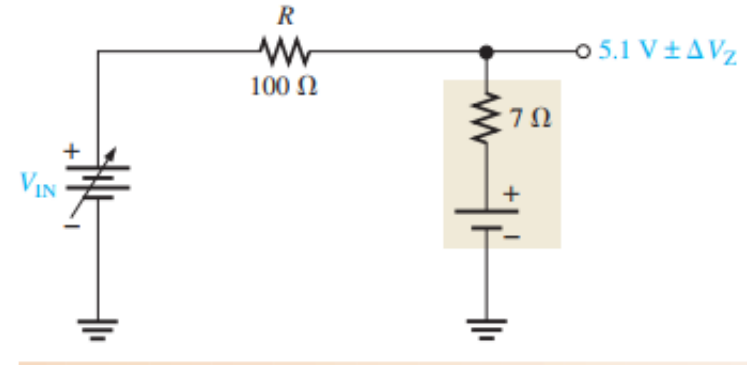


Fig 3.12 — Zener regulator for Example 3–5 Equivalent Circuit

Example 3-5 Solution Continued

At $I_{ZK} = 1 \text{ mA}$, the output voltage is

$$\begin{aligned} V_{\text{OUT}} &\cong 5.1 \text{ V} - \Delta V_Z = 5.1 \text{ V} - (I_Z - I_{ZK})Z_Z = 5.1 \text{ V} - (49 \text{ mA} - 1 \text{ mA})(7 \Omega) \\ &= 5.1 \text{ V} - (48 \text{ mA})(7 \Omega) = 5.1 \text{ V} - 0.336 \text{ V} = 4.76 \text{ V} \end{aligned}$$

Therefore,

$$V_{\text{IN}(\text{min})} = I_{ZK}R + V_{\text{OUT}} = (1 \text{ mA})(100 \Omega) + 4.76 \text{ V} = \mathbf{4.86 \text{ V}}$$

To find the maximum input voltage, first calculate the maximum zener current. Assume the temperature is 50°C or below; so from Figure 3-7, the power dissipation is 1 W.

$$I_{ZM} = \frac{P_D}{V_Z} = \frac{1 \text{ W}}{5.1 \text{ V}} = 196 \text{ mA}$$

At I_{ZM} , the output voltage is

$$\begin{aligned} V_{\text{OUT}} &\cong 5.1 \text{ V} + \Delta V_Z = 5.1 \text{ V} + (I_{ZM} - I_Z)Z_Z \\ &= 5.1 \text{ V} + (147 \text{ mA})(7 \Omega) = 5.1 \text{ V} + 1.03 \text{ V} = 6.13 \text{ V} \end{aligned}$$

Therefore,

$$V_{\text{IN}(\text{max})} = I_{ZM}R + V_{\text{OUT}} = (196 \text{ mA})(100 \Omega) + 6.13 \text{ V} = \mathbf{25.7 \text{ V}}$$

Zener Regulation with a Variable Load

• The Circuit

- Now the input is fixed, but the load resistor R_L across the zener can change

• How It Holds

- The total current through R_L stays about constant while the zener regulates
- The zener and the load share that current — whatever the load doesn't take, the zener does
- Regulation holds as long as I_Z stays between I_{ZK} and I_{ZM}

• From No Load to Full Load

- With the output open ($R_L = \infty$), the load takes no current — all of it flows through the zener
- Connect R_L : the current splits, part through the load (I_L) and part through the zener (I_Z)
- As R_L decreases, I_L increases and I_Z decreases (the total through R barely changes)
- Regulation continues until I_Z falls to I_{ZK} — that's the maximum load (full-load) the zener can support

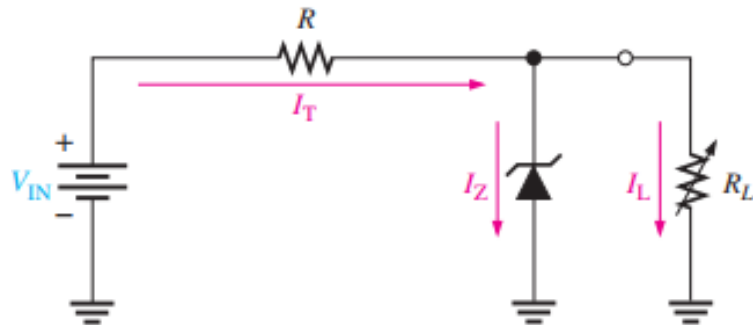


Fig 3.13 — Zener regulation with a variable load.

Worked Example — No Load to Full Load

• The Question

Determine the minimum and the maximum load currents for which the zener diode in Figure 3–14 will maintain regulation. What is the minimum value of R_L that can be used? $V_Z = 12\text{ V}$, $I_{ZK} = 1\text{ mA}$, and $I_{ZM} = 50\text{ mA}$. Assume an ideal zener diode where $Z_Z = 0\text{ }\Omega$ and V_Z remains a constant 12 V over the range of current values, for simplicity.

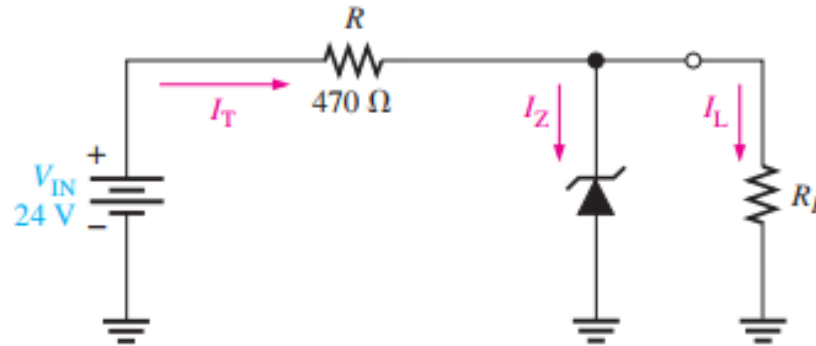


Fig 3.14 — Regulator circuit for the no-load to full-load example.

Worked Example — No Load to Full Load Continued

When $I_L = 0 \text{ A}$ ($R_L = \infty$), I_Z is maximum and equal to the total circuit current I_T .

$$I_{Z(\max)} = I_T = \frac{V_{\text{IN}} - V_Z}{R} = \frac{24 \text{ V} - 12 \text{ V}}{470 \text{ } \Omega} = 25.5 \text{ mA}$$

If R_L is removed from the circuit, the load current is 0 A. Since $I_{Z(\max)}$ is less than I_{ZM} , 0 A is an acceptable minimum value for I_L because the zener can handle all of the 25.5 mA.

$$I_{L(\min)} = \mathbf{0 \text{ A}}$$

The maximum value of I_L occurs when I_Z is minimum ($I_Z = I_{ZK}$), so

$$I_{L(\max)} = I_T - I_{ZK} = 25.5 \text{ mA} - 1 \text{ mA} = \mathbf{24.5 \text{ mA}}$$

The minimum value of R_L is

$$R_{L(\min)} = \frac{V_Z}{I_{L(\max)}} = \frac{12 \text{ V}}{24.5 \text{ mA}} = \mathbf{490 \text{ } \Omega}$$

Worked Example — Load Regulation with Zener Impedance

For the circuit in Figure 3–15:

- (a) Determine V_{OUT} at I_{ZK} and at I_{ZM} .
- (b) Calculate the value of R that should be used.
- (c) Determine the minimum value of R_L that can be used.

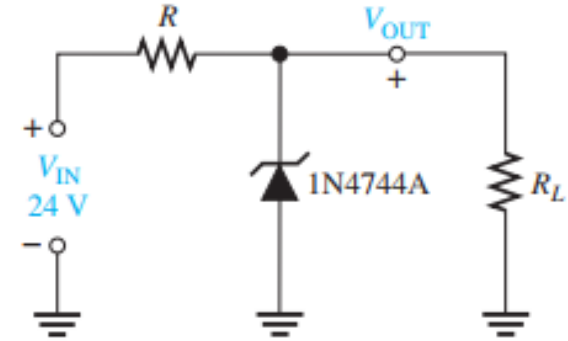


Fig 3.15 — Regulator circuit for the load-regulation example (zener impedance included).

Worked Example Solution — Load Regulation with Zener Impedance

The 1N4744A zener used in the regulator circuit of Figure 3–15 is a 15 V diode. The datasheet in Figure 3–7 gives the following information:

$V_Z = 15 \text{ V}$ @ $I_Z = 17 \text{ mA}$, $I_{ZK} = 0.25 \text{ mA}$, and $Z_Z = 14 \Omega$.

(a) For I_{ZK} :

$$\begin{aligned} V_{\text{OUT}} &= V_Z - \Delta I_Z Z_Z = 15 \text{ V} - \Delta I_Z Z_Z = 15 \text{ V} - (I_Z - I_{ZK}) Z_Z \\ &= 15 \text{ V} - (16.75 \text{ mA})(14 \Omega) = 15 \text{ V} - 0.235 \text{ V} = \mathbf{14.76 \text{ V}} \end{aligned}$$

Calculate the zener maximum current. The maximum power dissipation is 1 W.

$$I_{ZM} = \frac{P_D}{V_Z} = \frac{1 \text{ W}}{15 \text{ V}} = 66.7 \text{ mA}$$

For I_{ZM} :

$$\begin{aligned} V_{\text{OUT}} &= V_Z + \Delta I_Z Z_Z = 15 \text{ V} + \Delta I_Z Z_Z \\ &= 15 \text{ V} + (I_{ZM} - I_Z) Z_Z = 15 \text{ V} + (49.7 \text{ mA})(14 \Omega) = \mathbf{15.7 \text{ V}} \end{aligned}$$

(b) Calculate the value of R for the maximum zener current that occurs when there is no load as shown in Figure 3–16(a).

$$R = \frac{V_{\text{IN}} - V_{\text{OUT}}}{I_{ZK}} = \frac{24 \text{ V} - 15.7 \text{ V}}{66.7 \text{ mA}} = 124 \Omega$$

$R = \mathbf{130 \Omega}$ (nearest larger standard value), which reduces I_{ZM} to 63.8 mA.



Worked Example Solution — Load Regulation with Zener Impedance

(c) For the minimum load resistance (maximum load current), the zener current is minimum ($I_{ZK} = 0.25 \text{ mA}$) as shown in Figure 3–16(b).

$$I_T = \frac{V_{IN} - V_{OUT}}{R} = \frac{24 \text{ V} - 14.76 \text{ V}}{130 \text{ } \Omega} = 71.0 \text{ mA}$$

$$I_L = I_T - I_{ZK} = 71.0 \text{ mA} - 0.25 \text{ mA} = 70.75 \text{ mA}$$
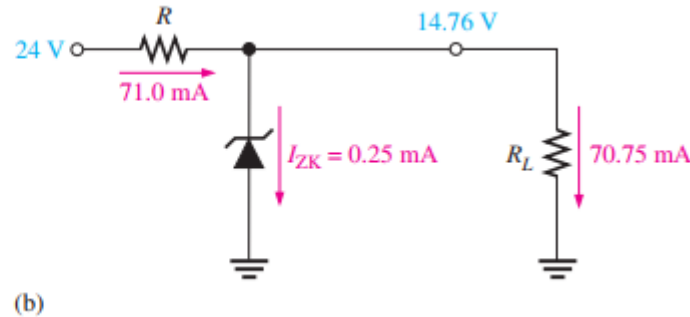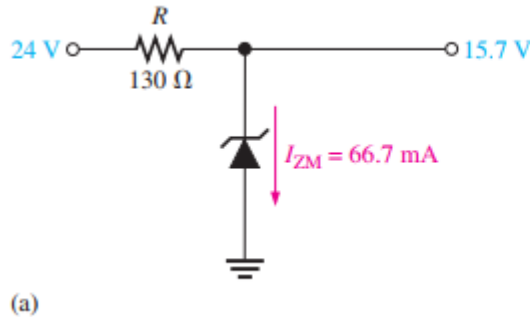
$$R_{L(\min)} = \frac{V_{OUT}}{I_L} = \frac{14.76 \text{ V}}{70.75 \text{ mA}} = \mathbf{209 \text{ } \Omega}$$



Zener Diode Limits

• Where the Zener Falls Short

- It wastes current and handles only modest loads — its load range is limited by I_{ZK} and I_{ZM}
- For tighter regulation and larger loads, a transistor or IC regulator is used (built around a zener reference)
- Zeners also serve as simple limiters/clippers, capping a waveform near V_Z

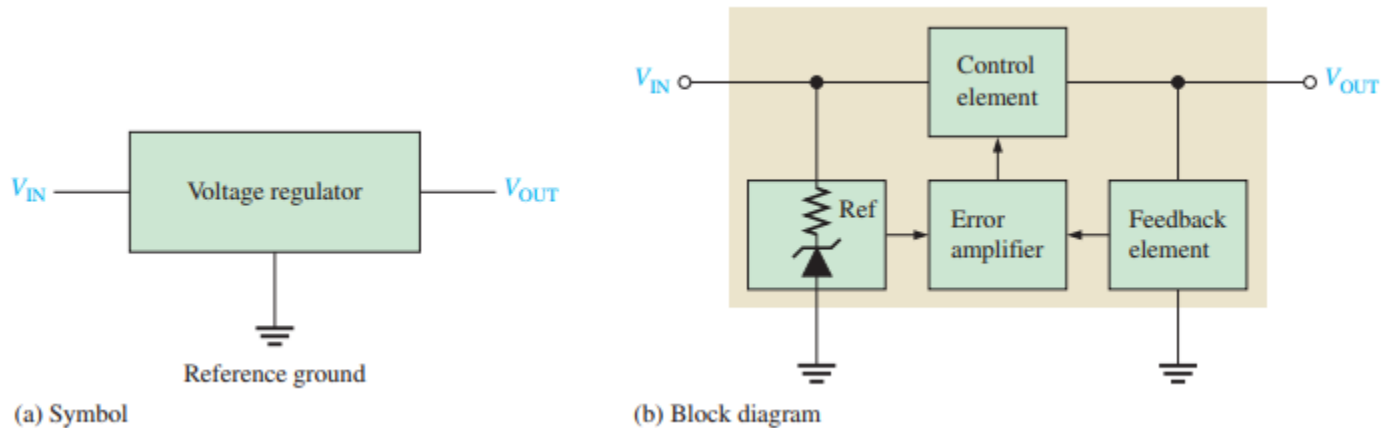


Fig 3.17 — Three-terminal voltage regulators

Quick Check #2 — Zener Regulation

- **Question 1**

- In input regulation, what changes as V_{IN} varies, and what sets the input limits?

- **Question 2**

- Why are zener regulators best suited to low-current loads?

- **Question 3**

- In load regulation, what happens to I_z as the load current I_L increases?

- **Question 4**

- What defines the full-load condition for a zener regulator?

- **Question 5**

- For $V_{IN} = 20\text{ V}$, $V_Z = 10\text{ V}$, $R = 220\ \Omega$, what is the total current through R ?

Part 3 — Wrap-Up

When to use a Zener Diode

- **Good Fit**

- You need a stable, low-cost voltage reference (e.g. for a meter or a bias point)
- You need to regulate a small load where efficiency isn't critical

- **Mind the Limits**

- Keep I_Z between I_{ZK} and I_{ZM} , and keep P_D below the (derated) maximum
- Pick V_Z for the voltage you want, and the series R to set the current

- **When to Move On**

- For higher current or tighter regulation, use an IC/transistor regulator — often with a Zener diode inside as the reference

Key Takeaways from Today

- A zener diode is built to operate in reverse breakdown, where V_z stays nearly constant as I_z changes
- Zener breakdown dominates below ~ 5 V (heavy doping, thin junction); avalanche dominates above ~ 5 V
- It regulates only between I_{zK} (knee) and I_{zM} (max); V_z is quoted at a test current
- Practical model adds zener impedance: $Z_z = \Delta V_z / \Delta I_z$ — keep away from the knee
- Temperature: $\Delta V_z = V_z \cdot TC \cdot \Delta T$. Power: $PD = V_z \cdot I_z$, derated above the rated temperature
- Input regulation: as V_{IN} varies, I_z absorbs the change (range set by I_{zK} and I_{zM})
- Load regulation: Zener and load share the total current; as I_L rises, I_z falls — full load is reached at I_{zK}

Coming Up — Week 7: Special-Purpose Diodes

- **Next Topic — Special-Purpose Diodes (Lecture Notes pp. 90–116)**

- The varactor (voltage-variable capacitance) and its tuning applications
- Optical diodes: the LED and the photodiode
- A survey of other special diodes (Schottky, PIN, current-regulator, step-recovery, and more)

- **To Prepare**

- Keep the diode V-I picture in mind — each special diode tweaks one part of it

- **Reminder**

- Read pp. 90–116 before class

Thank You — Questions?